




Quiz 7

* Full Name

* WISH Participant ID

701. At a frequency of 100 rad/sec, V_{out} is -46 dB with respect to V_{in} . The value of R is equal to:

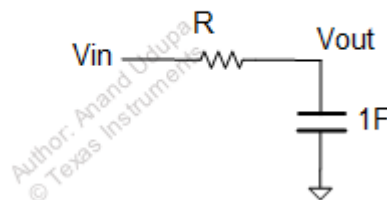- (a) 100Ω
- (b) 4Ω
- (c) 1Ω
- (d) 2Ω
- (e) 200Ω
- (f) 10Ω
- (g) 20Ω
- (h) 5Ω



Answer the Question 701

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

702. With respect to V_{in} , V_{out} is -32 dB lower at 100 rad/sec and -52 dB lower at 10,000 rad/sec. The value of R and C are:

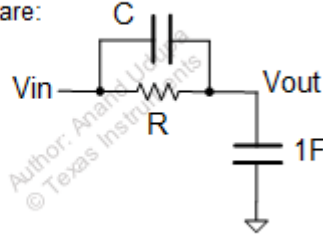- (a) 160Ω , 2.5 mF
- (b) 0.4Ω , 2.5 mF
- (c) $2.5\mu\Omega$, 400F
- (d) 2.5Ω , 1F
- (e) 10Ω , 1F
- (f) 40Ω , 1 mF
- (g) 4Ω , 20 mF
- (h) Insufficient information




Answer the Question 702

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

703. For input at A, output at D, the pole location is:

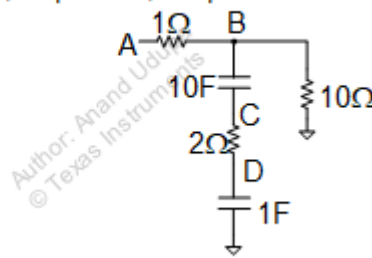- (a) 1.2 rad/s
- (b) 0.63 rad/s
- (c) 0.55 rad/s
- (d) 1 rad/s
- (e) 4.24 rad/s
- (f) 6.36 rad/s
- (g) 0.38 rad/s
- (h) 0.22 rad/s



Answer the Question 703

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

704. In circuit of Q3: For input at B, output at D, the pole location is:

- (a) 1.2 rad/s
- (b) 1 rad/s
- (c) 0.05 rad/s
- (d) 0.38 rad/s
- (e) 0.55 rad/s
- (f) 0.63 rad/s
- (g) 0.46 rad/s
- (h) 0.22 rad/s


Author: Anand Udupa
© Texas Instruments

Answer the Question 704

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

706. A1 and A2 are ideal buffers with gain of 2 and 5 respectively. Magnitude of V_{out} with respect to V_{in} at a frequency of 100 rad/s is:

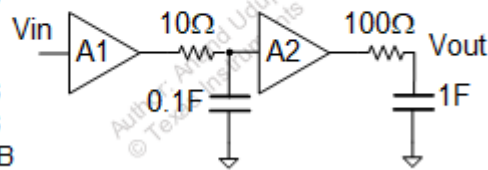- (a) -40 dB
- (b) -50 dB
- (c) 0 dB
- (d) 20 dB
- (e) -80 dB
- (f) -60 dB
- (g) -120 dB
- (h) -100 dB




Answer the Question 706

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

710. In the circuit shown below, the input is driven with a waveform $V_{IN}=1.u(t)$. At a time of 2ns, the voltage at V_{OUT} is roughly equal to:

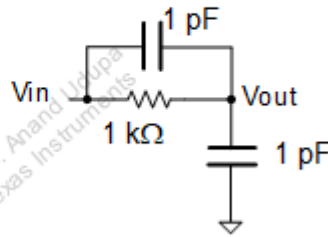- (a) 1 V
- (b) 0.315 V
- (c) 0.93 V
- (d) 0 V
- (e) 0.81 V
- (f) 0.5 V
- (g) 0.63 V
- (h) 0.99 V




Answer the Question 710

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

711. A sine wave of amplitude 1V and frequency 100 Grad/s is applied at V_{IN} . The amplitude at V_{OUT} is roughly equal to:

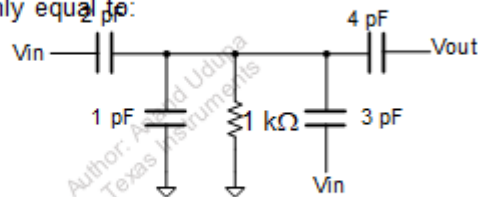- (a) 1 V
- (b) 0.33 V
- (c) 0.5 V
- (d) 0 V
- (e) 0.99 V
- (f) 0.25 V
- (g) 0.63 V
- (h) 0.83 V




Answer the Question 711

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

712. A 2-port electrical component is recovered from an alien space ship. After some characterization in the TI lab, it is found to have a characteristic of $i = (1e-3).v + (1e-6).dv/dt$, where i is the current through the component and v is the voltage across the component. The component (represented by the box below) is then used in a circuit as shown below. What will be the 3-dB bandwidth between $V_{in}(t)$ and $V_o(t)$?

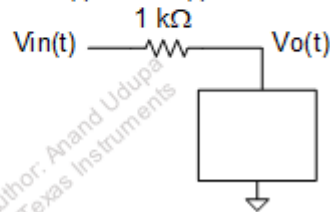- (a) 1 Krad/s
- (b) 500 rad/s
- (c) 100 rad/s
- (d) 2 Krad/s
- (e) 4 Krad/s
- (f) 250 rad/s
- (g) 10 Krad/s
- (h) Infinite



Answer the Question 712

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

713. A system has a DC gain of 3 and a gain at infinite frequency equal to 6. Which of the following statements is TRUE?

- (a) Number of poles is greater than number of zeros
- (b) Number of poles is equal to number of zeros
- (c) Number of poles is less than number of zeros
- (d) The system has neither poles nor zeros


Answer the Question 713

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |

☐ c☐ g☐ d☐ h

715. An oscilloscope probe has the RC model as shown below. What is the 3-dB bandwidth when it is hooked to the oscilloscope with a 1m cable?

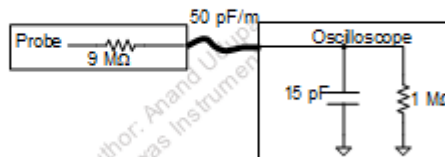- (a) 12.4 kHz
- (b) 17 kHz
- (c) 1.8 kHz
- (d) 0.26 kHz
- (e) 5.6 kHz
- (f) 10.2 kHz
- (g) 2.7 kHz
- (h) 11.7 kHz




Answer the Question 715

☐ a☐ e☐ b☐ f☐ c☐ g☐ d☐ h

717. The circuit shown below is an example of a differential sampling circuit. The input signal is a differential sine wave on VINP and VINM. VCM is a DC voltage. The phase where the 5 switches are ON is referred to as the sampling phase and during this phase, (VINP-VINM) gets stored as a voltage difference between the 2 capacitors. What is the 3 dB bandwidth of this circuit if the equivalent resistance of each of the switches is 100 Ohm

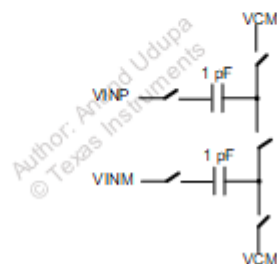- (a) 4 Grad/s
- (b) 10 Grad/s
- (c) 3.33 Grad/s
- (d) 1 Grad/s
- (e) 0.25 Grad/s
- (f) 7.5 Grad/s
- (g) 12.5 Grad/s
- (h) 5 Grad/s



Answer the Question 717

☐ a

☐ e

☐ b

☐ f

☐ c

☐ g

☐ d

☐ h

Done

Powered by



See how easy it is to [create surveys and forms](#).

[Privacy & Cookie Notice](#)