




Quiz 6

* Full Name

* WISH Participant ID

601. $V_s = 4.u(t)$. Voltage at Node X at $t = 1\text{sec}$ is:

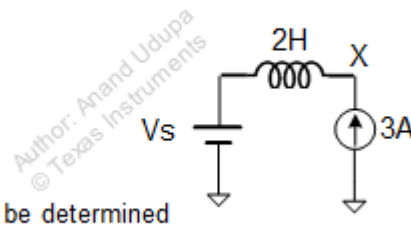- (a) 3V
- (b) 1V
- (c) Infinity
- (d) 1.5V
- (e) 6V
- (f) 0V
- (g) 4V
- (h) Cannot be determined



Answer the Question 601

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

602. $V_s = 3 + 4.u(t)$. Initial current through inductor (at $t=0^-$) is 1A. Current through inductor at $t=5\text{sec}$ is:

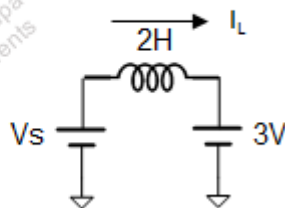- (a) 10A
- (b) 11A
- (c) 5A
- (d) 0A
- (e) 1A
- (f) 21A
- (g) 6A
- (h) ∞A




Answer the Question 602

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

608. $I_s = 3.r(t) - 3.r(t-5)$. Initial current through inductor is 0. Average power provided by the current source between $t=0\text{sec}$ and $t=4\text{sec}$ is:

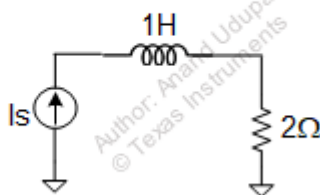- (a) 0V
- (b) 50W
- (c) 114W
- (d) 18W
- (e) 96W
- (f) 132W
- (g) 0W
- (h) 72W




Answer the Question 608

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

609. $I_s = 2.r(t)$ where $r(t)$ is a ramp function. $V_s = 3.r(t)$.
Voltage at Node X at time $t = 2.5\text{sec}$ is:

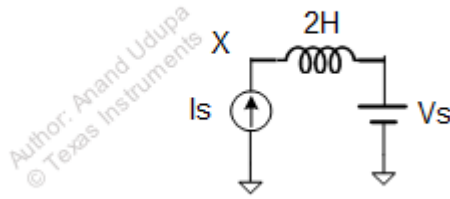- (a) 0V
- (b) 11.5V
- (c) 4V
- (d) 2V
- (e) 7V
- (f) 5V
- (g) 13.5V
- (h) 9.5V



Answer the Question 609

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

611. An inductor of value 1 Henry is driven with a periodic voltage waveform source across it. The average current through the source in steady state is measured to be 1A. The same voltage source is then connected across a 1F capacitor. The average current through the voltage source is now equal to:

- (a) 0 A
- (b) 2 A
- (c) 0.5 A
- (d) 1 A
- (e) 0.1 A
- (f) 10 A
- (g) 5 A
- (h) Some key information is missing


Answer the Question 611

- | | |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |

☐ d☐ h

612. An inductor is connected in series with a black box as shown below and the series combination is driven by a DC voltage source V_{in} . If the component inside the black box keeps the inductor current bounded, the black box cannot be which of the following components?

- (a) Capacitor
- (b) Resistor
- (c) An ideal current source
- (d) A voltage source equal to V_{in}
- (e) Open circuit
- (f) Reverse biased diode
- (g) R||C
- (h) A voltage controlled voltage source controlled by V_{in} with a gain of 2

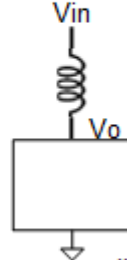

Answer the Question 612

☐ a☐ e☐ b☐ f☐ c☐ g☐ d☐ h

Done

Powered by



See how easy it is to [create surveys and forms](#).

[Privacy & Cookie Notice](#)